

Chapter 11

I/O Interfacing

- One type of instruction **transfers information** to an I/O device (**OUT**).
- Another **reads** from an I/O device (**IN**).
- Instructions are also provided to transfer strings of data between memory and I/O.
 - **INS** and **OUTS**, found except the 8086/8088

- Instructions that transfer data between an **I/O device** and the microprocessor's **accumulator** (AL, AX, or EAX) are called **IN** and **OUT**.
- The I/O address is stored in register DX as a 16-bit address or in the byte (p8) immediately following the **opcode** as an **8-bit address**.
 - Intel calls the **8-bit** form (p8) a **fixed address** because it is stored with the instruction, usually in a ROM
- The **16-bit address** is called a **variable address** because it is stored in a DX, and then used to address the I/O device.

Other instructions that use DX to address I/O are the **INS** and **OUTS** instructions.

- I/O ports are **8 bits** in width.
 - a **16-bit port** is actually **two** consecutive **8-bit ports** being addressed
 - a **32-bit I/O port** is actually **four 8-bit ports**

- When data are transferred using **IN** or **OUT**, the I/O address, (**port number** or simply port), appears on the address bus.
- External I/O interface decodes the **port** number in the same manner as a memory address.
 - the 8-bit fixed **port number** (p8) appears on address bus connections A_7-A_0 with bits $A_{15}-A_8$ equal to 00000000_2
 - connections above A_{15} are **undefined** for I/O instruction

- The 16-bit variable **port number** (DX) appears on address connections $A_{15}-A_0$.
- The first **256 I/O port** addresses (00H–FFH) are accessed by both fixed and variable I/O instructions.
 - any I/O address from 0100H to FFFFH is only accessed by the variable I/O address

- **INS** and **OUTS** instructions address an I/O device using the DX register.
 - but do not transfer data between accumulator and I/O device as do the IN/OUT instructions
 - Instead, they **transfer data** between memory and the I/O device.

- Two different methods of interfacing I/O: **isolated I/O** and **memory-mapped I/O**.
- In **isolated I/O**, the IN, INS, OUT, and OUTS transfer data between the microprocessor's **accumulator** or memory and the **I/O device**.
- In memory-mapped I/O, any instruction that references memory can accomplish the transfer.
- The PC does not use memory-mapped I/O.

ISOLATED I/O

- The most common I/O transfer technique used in the **Intel-based system** is **isolated I/O**.
 - *isolated* describes how I/O locations are isolated from memory in a separate I/O address space
- Addresses for **isolated I/O devices**, called **ports**, are separate from memory.
- Because the ports are separate, the user can expand the memory to its full size without using any of **memory space** for **I/O devices**.


- A disadvantage of isolated I/O is that data transferred between I/O and microprocessor must be accessed by the **IN**, **INS**, **OUT**, and **OUTS** instructions.
- **Separate control signals** for the I/O space are developed.

Memory-Mapped I/O

- Memory-mapped I/O does not use the IN, INS, OUT, or OUTS instructions.
- It uses any instruction that transfers data between the microprocessor and memory.
 - treated as a memory location in memory map
- Advantage is any memory transfer instruction can access the I/O device.
- Disadvantage is a portion of memory system is used as the I/O map.
 - reduces memory available to applications

Basic Input and Output Interfaces

 - The basic **input device** is a set of **three-state buffers**.
- The basic **output device** is a set of **data latches**.
- The term **IN** refers to moving data *from the I/O device into* the microprocessor and
- The term **OUT** refers to moving data *out of the microprocessor to* the I/O device.




The Basic Input Interface

- Three-state buffers are used to construct the 8-bit input port.
- External data are connected to the inputs of the buffers, buffer outputs connect to the data bus.
- The circuit of allows the processor to read the contents of the eight switches that connect to any 8-bit section of the data bus when the select signal becomes a logic 0.
- When the IN instruction executes, contents of the switches copy to the AL register.

The Basic Output Interface

 - Receives data from the processor and usually must hold it for some external device.
- 8 light-emitting diodes (LEDs) connect to the processor through a set of eight data latches.
- The latch stores the number output by the microprocessor from the data bus so that the LEDs can be lit with any 8-bit binary number.



- Latches **hold** the data because when the processor executes an OUT, data are only present on the data bus for less than $1.0\ \mu\text{s}$.
 - the viewer would never see the LEDs illuminate
- When the OUT executes, data from AL, AX, or EAX transfer to the latch via the data bus.
- Each time the OUT executes, the SEL signal activates, **capturing data** to the latch.
 - data are held until the next OUT
- When the output instruction is executed, data from the **AL register** appear on the LEDs.

Handshaking

- Many I/O devices accept or release information **slower** than the microprocessor.
- A method of I/O control called **handshaking** or **polling**, synchronizes the I/O device with the microprocessor.
- An example is a parallel printer that prints a few hundred characters per second (**CPS**).
- The processor can send data much **faster**.
 - a way to slow the microprocessor down to match speeds with the printer must be developed
 - the printer receives data, it places logic 1 on the **BUSY** pin, indicating it is printing data, **BUSY** indicates the printer is busy

- The software **polls** or tests the **BUSY** pin to decide whether the printer is busy.
 - If the **printer** is **busy**, the **processor waits**
 - if not, the next ASCII character goes to the printer
- This process of interrogating the printer, or any asynchronous device like a printer, is called **handshaking** or **polling**.

I/O PORT ADDRESS DECODING

- Very **similar** to memory address decoding, especially for memory-mapped I/O devices.
- The difference between memory decoding and isolated I/O decoding is the number of address pins connected to the decoder.

Decoding 8-Bit I/O Port Addresses

- Fixed I/O instruction uses an 8-bit I/O port address that on $A_{15}-A_0$ as 0000H–00FFH.
 - we often decode only address connections A_7-A_0 for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an 8-bit address, we can never include I/O devices using a 16-bit address.

Decoding 16-Bit I/O Port Addresses

- The difference between decoding an 8-bit and a 16-bit I/O address is that eight additional address lines (A_{15} – A_8) must be decoded

- Data transferred to an 8-bit I/O device exist in one of the I/O banks in a **16-bit processor** such as 80386SX.
- The I/O system on such a microprocessor contains **two 8-bit memory banks**.
- Because two I/O banks exist, any 8-bit I/O write requires a **separate write**.
- I/O reads don't require **separate strobes**.
 - as with memory, the processor reads only the byte it expects and ignores the other byte
 - a read can cause problems when an I/O device responds incorrectly to a read operation.

THE PROGRAMMABLE PERIPHERAL

- 82C55 **programmable peripheral interface (PPI)** is a popular, low-cost interface component found in many applications.
- The PPI has **24 pins for I/O**, programmable in groups of 12 pins and groups that operate in three distinct modes of operation.
- 82C55 can interface any **I/O device** to the **microprocessor**.

Description of the 82C55

- The **three I/O ports** (labeled **A**, **B**, and **C**) are programmed as groups.
 - **group A** connections consist of **port A** (PA_7 – PA_0) and the **upper half** of **port C** (PC_7 – PC_4)
 - **group B** consists of **port B** (PB_7 – PB_0) and the **lower half** of **port C** (PC_3 – PC_0)
- 82C55 is selected by its CS' pin for programming and reading/writing to a port.

82C55

26

